

# Experiment 2 - Frequency Regulation

Ali Bahari,  
810196688

**Abstract**— This document gives the final results of the second experiment of digital logic design laboratory.

## I. INTRODUCTION

The goal of this experiment is to design an adjustable clock generator that can fix the output frequency at the desired value meaning that we will construct a component which by changing the initial values of the frequency divider that was created in the last experiment gradually, can generate the desirable frequency at the end. Finally in the end it's tested and shown that using FPGA and setting the correct parallel loads for frequency divider will result in desired frequency.

## II. DESIGN DESCRIPTION AND SYNTHESIS

In this part we will make and code the component that was mentioned above.

1. The code is provided in the sent files under the folder named 1. In the code everything is done by the help of instructions in the experiment.
2. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus.
3. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus.
4. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus. Also 74LS191 is changed in this experiment and is replaced by 74LS193 as mentioned in the experiment's description.
5. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus.
6. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus. There is input by the name FPGA\_clk for this purpose and it'll receive 50 MHz clock signal in the test bench.
7. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus.
8. Done in Quartus. The files for Quartus is provided in sent files under the folder named 1 Quartus.

## III. DESIGN SIMULATION IN MODELSIM

In this part we are going to test the design so to understand whether it is working correctly or not. Also the circuit is brought into Modelsim from Quartus.

1. Test bench is provided in sent files under the folder named 1 ModelSim and there are descriptions in the code commented as well for any needed clarification. In

the test bench ring oscillator code is provided by TA and it is used for frequency divider clock. Also in the test bench there is a 50 MHz clock signal for FPGA, since the frequency is 50 MHz so clock cycle length will be 20 ns. Other components are also placed correctly for testing such as FPGA, ring oscillator, FPGA\_clk and so on. Also there is an AND gate for frequency divider load so that we can set load value for divider like the last experiment.

2. The results are shown below in Table 1.

TABLE I  
ACHIEVED RESULTS FOR DIFFERENT RING OSCILLATOR FREQUENCIES

Ring Oscillator Frequency	Desired Frequency	Final Parallel Loads	Initial Parallel Loads	SetPeriod
20000 KHz (clock = 50 ns)	400 KHz	205	127	125
20080 KHz (clock = 49.8 ns)	400 KHz	205	127	125
19841 KHz (clock = 50.4 ns)	400 KHz	205	127	125
20550 KHz (clock = 48.66 ns)	400 KHz	205	127	125
20375 KHz (clock = 49.08 ns)	400 KHz	205	127	125
19960 KHz (clock = 50.1 ns)	400 KHz	205	127	125
19912 KHz (clock = 50.22 ns)	400 KHz	205	127	125

Since the experiment description states that the desired frequency must be 400 KHz and also FPGA frequency must be 50 MHz at all times, setPeriod will always be 125. Also in FPGA code the initial parallel loads always start from 127 and must reach 205 because setPeriod is always the same. Ring oscillator frequency is changed by a small amount for multiple tests as shown above, frequency is shown clearly and also clock parameter in Table 1 shows the clock cycle length of ring oscillator, this parameter is changed in ring oscillator code by changing INV\_DELAY\_ns which is delay of each inverter and

since there are three inverters this parameter will equal clock values in Table 1 divided by 6.

3. All the waveforms are provided below in figures 1 to 6. In some of the waveforms since the exact frequency is not reachable, it'll fluctuate between increasing and decreasing but the final loads will always be 205 and it'll be centred on it. That is the reason for some of the figures fluctuating between increase and decrease when FPGA reaches the end result. But in some cases since there is a part for being equal in the code the end result will exactly be 205 and there won't be any fluctuation.

 


Fig. 1 All the wanted waveforms for ring oscillator with frequency 20080 KHz (49.8 ns)

 


Fig. 2 All the wanted waveforms for ring oscillator with frequency 19841 KHz (50.4 ns)

 


Fig. 3 All the wanted waveforms for ring oscillator with frequency 20550 KHz (48.66 ns)

 


Fig. 4 All the wanted waveforms for ring oscillator with frequency 20375 KHz (49.08 ns)

 


Fig. 5 All the wanted waveforms for ring oscillator with frequency 19960 KHz (50.1 ns)

 


Fig. 6 All the wanted waveforms for ring oscillator with frequency 19912 KHz (50.22 ns)